

Task 3

In this section, is implemented a Moore's state machine already defined, as shown below.

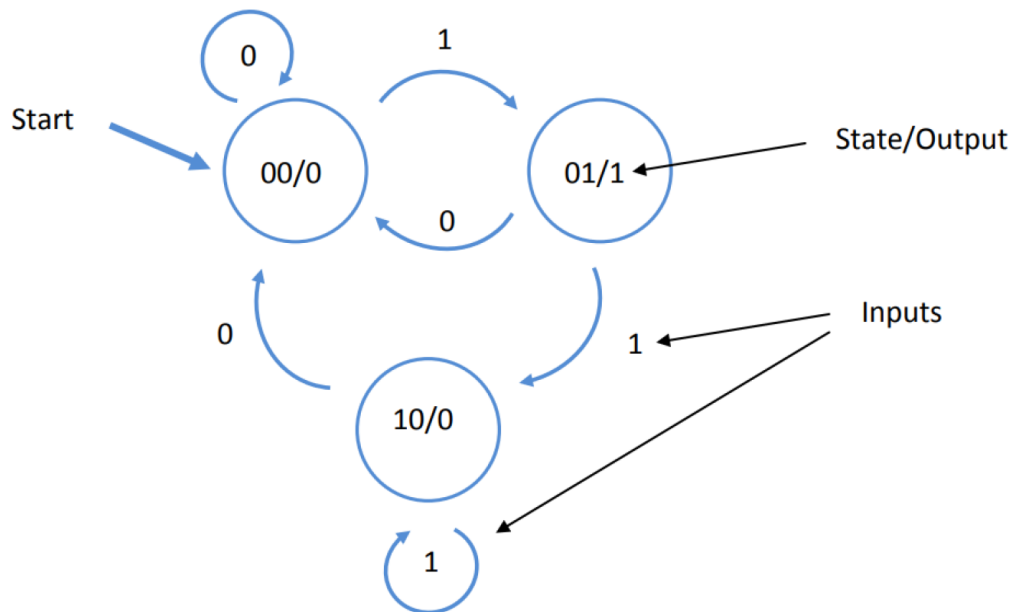


Figure 1: Moore state machine diagram

Using the diagram, the following table of transitions is made.

Estado Actual		Estado Siguiente		Salidas
	y2 - y1	W		Z
		0	1	
A	00	A	B	0
B	01	A	C	1
C	10	A	C	0

Figure 2: Moore state machine - Transitions

With the transitions, using Karnaugh's maps, the functions for the states and the output are made as shown below.

		y2y1			
		00	01	11	10
W	0	0	0	X	0
	1	0	1	X	1

		y2y1			
		00	01	11	10
W	0	0	0	0	1
	1	1	0	1	0

Figure 3: Maps for Y_2 (left) and Y_1 (right) functions.

Where $Y_2 = W \cdot y_1 + W \cdot y_2$, and $Y_1 = W \cdot \overline{y_2} \cdot \overline{y_1}$. From the transitions table, it is simple to see that $Z = y_1$. With the functions, the state machine is implemented using two D Flip Flops as follows.

 


Figure 4: Moore state machine - Circuit implementation

Now the same system is implemented using a Mealy's state machine, with resulting diagram is shown below.

 


Figure 5: Mealy state machine diagram

Notice that it requires one less state than Moore's machine because of the direct connection of the from the input to the output. The following transition table is made using the diagram.

Estado Actual		Estado Siguiente		Salidas	
	y	W		Z	
		0	1	W=0	W=1
A	0	A	B	0	1
B	1	A	B	0	0

Figure 6: Mealy state machine - Transitions

With the table, using Karnaugh's maps, are made the functions for the states and the output.

y	W	
	0	1
0	0	1
1	0	1

y	W	
	0	1
0	0	1
1	0	0

Figure 7: Maps for Y (left) and Z (right)

Where from the left map $Y = W$, and from the right table $Z = \bar{y} \cdot W$. With the defined functions, the state machine is implemented using one D Flip Flop as shown below.

 


Figure 8: Mealy state machine - Circuit implementation

Since the internal logic works with 3.3V power supply, and the external signals work with 5V, level shifters are implemented using BJT transistors. For adapting the inputs of CLK and W, the circuits are shown below.

 


Figure 9: Level shifter for CLK from 5V to 3.3V (VCC)

 


Figure 10: Level shifter for W from 5V to 3.3V (VCC). The inverting gate is to compensate the transistor logic inversion.

And for the outputs (Moore and Mealy machines) the driver circuit is as shown below.

 


Figure 11: Driver for LED output.

The design of the circuits with the corresponding calculations are included in the *Annex*.

Annex

Level shifter for inputs

From the implemented circuit:

 


Figure 12: Level shifter for CLK from 5V to 3.3V (VCC)

Usign for $I_{SAT} = 1\text{ mA}$, considering $VCE_{SAT} = 0.2\text{ V}$, the equation from the out mesh:

$$3.3\text{ V} - VCE_{SAT} - I_{SAT}R_1 = 0$$

$$\frac{3.3\text{ V} - VCE_{SAT}}{I_{SAT}} = R_1 = 3.1\text{ K}\Omega$$

Normalizing we have $R_1 = 3.3\text{ K}\Omega$. Considering $HFE_{MIN} = 100$, from the input mesh:

$$5\text{ V} - VBE_{ON} - \frac{I_C}{HFE_{MIN}}R_2 = 0$$

$$\frac{5\text{ V} - VBE_{ON}}{I_C}HFE_{MIN} = R_2 = 430\text{ K}\Omega$$

Normalizing we have $R_2 = 390\text{ K}\Omega$.

Driver for output led

Taking the implemented circuit:

 


Figure 13: Driver for LED output.

Usign for $I_{LED} = 10mA$, considering $VCE_{SAT} = 0.2V$ and $V_{LED} = 2V$, the equation from the out mesh:

$$3.3V - V_{LED} - VCE_{SAT} - I_{LED}R_3 = 0$$

$$\frac{3.3V - V_{LED} - VCE_{SAT}}{I_{LED}} = R_3 = 110\Omega$$

Normalizing we have $R_3 = 220\Omega$. Considering $HFE_{MIN} = 100$, from the input mesh:

$$3.3V - V_{BE_{ON}} - \frac{I_C}{HFE_{MIN}}R_4 = 0$$

$$\frac{3.3V - V_{BE_{ON}}}{I_C}HFE_{MIN} = R_4 = 26K\Omega$$

Normalizing we have $R_4 = 22K\Omega$, to guarantee saturation.